

Q What is diff b/w universal gate & basic gates
 Q Explain AND gate, NOR gate, NOT gate with logic diagram & truth table.

Ans: 1 Basic logic gates are used in operation in digital systems. Types of Basic logic gates are:-

- OR Gate
- NOT Gate
- AND Gate
- XOR Gate

Through these gates we can perform all basic arithmetic functions like addition, multiplication, etc can be realized.

Q.2 OR gate


Input		Output
A	B	$A \text{ OR } B$
0	0	0
0	1	1
1	0	1
1	1	1

Universal Gate:


It is a gate which includes NAND gate and NOR gate as thought. These gates all other gates can be realized from these gates.

Example NAND gate

Input		Output
A	B	\overline{AB}
0	0	1
0	1	1
1	0	1
1	1	0

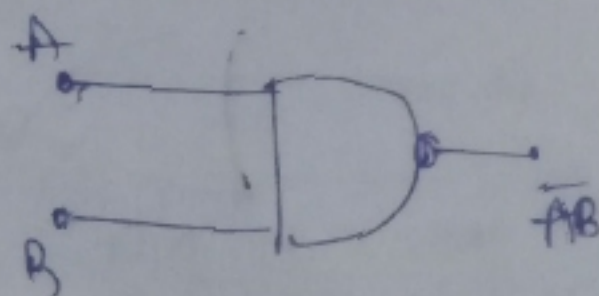

Ans 23 AND Gate:-

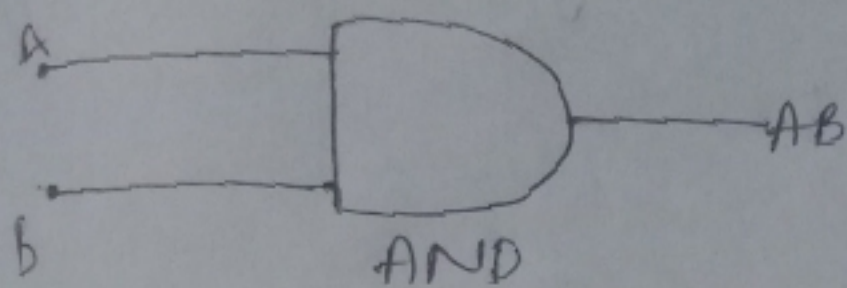


Input		Output
A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

AND gate is electronic circuit, it takes 2 input, A dot (\cdot) is used to show the AND operation i.e. $(A \cdot B)$

It gives a high output (i.e. 1) only if all the input are high

NOT Gate

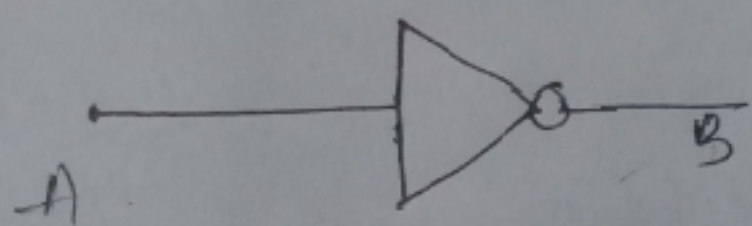


Input	Output
A	\bar{A}
0	1
1	0

Input	Output
A	\bar{A}
0	1
1	0

This gate is also known as inverter. If the input variable is A, the inverted output is known as NOT A, or A' or \bar{A} .

NOR Gate

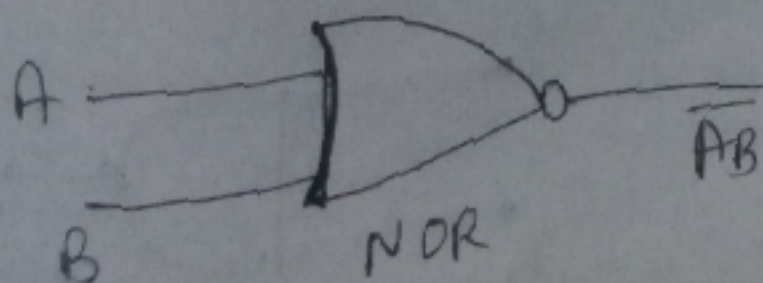

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

This is a NOT-OR gate which is equal
to an OR gate followed by a NOT gate
The outputs of all NOR gates are low
if any of the inputs are high.